

BBM233: Logic Design Lab
2024 Fall
Lab Experiment 1 Report

Sinan Ermiş, 2220356143

October 14, 2024

1 Question 1

Table 1: Truth Table

T	A	F	Output
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

2 Question 2

Boolean function: $Dispense_Food(T, A, F) = (T \wedge F) \vee (\neg T \wedge A \wedge F)$

3 Question 3

Circuit implementation:

